

## GCSE Physics AQA Topic 2




- Triple Science Content only in purple
- Triple Science and Higher Content Only in blue


## 2. Electricity

### 2.1 Current, Potential Difference, and Resistance
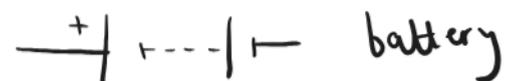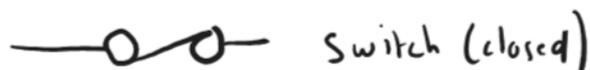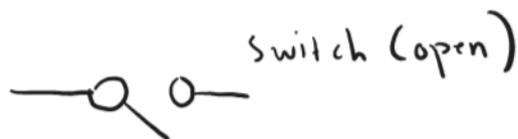
#### 2.1.1 Standard Circuit Diagram Symbols:

- Recognize symbols for components like **cells**, **batteries**, **resistors**, **lamps**, **switches**, **ammeters**, and **voltmeters**.
  - Circuit diagrams show how components are connected and how current flows.



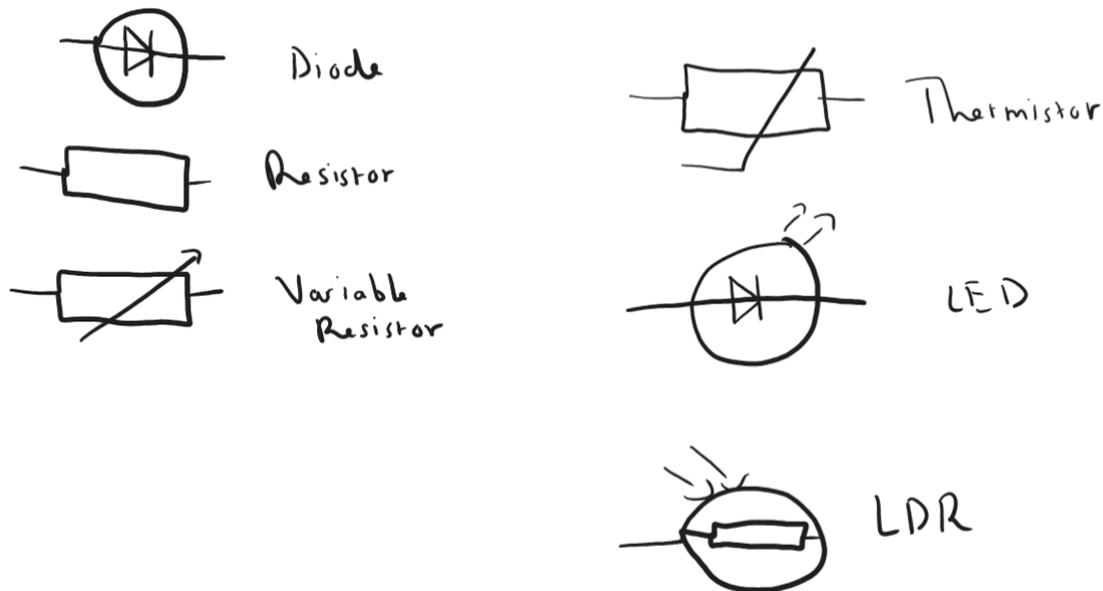

### Electrical Charge and Current:

- **Electric current** is the flow of charge through a conductor. It is only possible in a closed circuit with a source of potential difference (voltage).
- The **size of the current** depends on the rate of flow of electrical charge, measured in **amperes (A)**.
- $Q = It$   
Where:
  - $Q$  = charge (in coulombs, C),
  - $I$  = current (in amperes, A),
  - $t$  = time (in seconds).

### Current, Resistance, and Potential Difference:

- The **current** through a component depends on two things:
  - The **resistance** of the component.
  - The **potential difference (voltage)** across it.
- The greater the resistance, the smaller the current for a given potential difference.
- $V = IR$ :  
Where:
  - $V$  = potential difference (volts),
  - $I$  = current (amperes),
  - $R$  = resistance (ohms,  $\Omega$ ).

## Resistors:

- **Ohmic conductors** (e.g., metal wires) have a constant resistance at a constant temperature, so the current is proportional to the potential difference.
- **Non-ohmic components** have changing resistance depending on conditions:
  - **Filament lamps:** Resistance increases as the filament gets hotter.
  - **Diodes:** Only allow current to flow in one direction and have high resistance in the reverse direction.
  - **Thermistors:** Resistance decreases as temperature increases.
  - **LDRs (Light Dependent Resistors):** Resistance decreases as light intensity increases.

## Series and Parallel Circuits

- **Series Circuits:**
  - Components are connected in a single path.
  - The current is the same through each component.
  - The total resistance is the sum of all the individual resistances:

$$R_{total} = R_1 + R_2 + \dots + R_{total}$$

- **Parallel Circuits:**
  - Components are connected in separate branches.
  - The potential difference is the same across each branch.
  - The total current is the sum of the currents through each branch.
  - The total resistance is less than the resistance of the smallest resistor:

$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_{total}}$$

## Direct and Alternating Current:

- **Direct current (DC):** Current flows in one direction only (e.g., from batteries).
- **Alternating current (AC):** Current constantly changes direction.
  - UK mains electricity is **AC** with a frequency of **50 Hz** and a voltage of **230 V**.

## Mains Electricity:

- Electrical appliances are connected to the mains using **three-core cables**:
  - **Live wire (brown)** – carries **230 V AC** from the supply. Dangerous even when switch is off.
  - **Neutral wire (blue)** – completes the circuit and carries current **away**.
  - **Earth wire (green/yellow)** – a **safety wire** that prevents electric shock by directing current to the ground if the case becomes live.

## Safety Features

- **Fuses** melt if too much current flows → breaks the circuit.
- **Circuit breakers (RCCBs)** detect differences in current between live and neutral and cut off supply instantly.
- **Double insulation** – devices with plastic casings don't need an earth wire.

## Energy Transfers

### 2.4.1 Power:

- **Power** is the rate at which energy is transferred or work is done.
  - Formula:
- $P = IV$   
Where:
  - $P$  = power (watts, W),

- $V$  = potential difference (volts, V),
- $I$  = current (amperes, A).
- Another formula for power (using resistance):
- $P = I^2 R$   
Where:
  - $P$  = power (watts, W),
  - $I$  = current (amperes, A),
  - $R$  = resistance (ohms,  $\Omega$ ).

### Energy Transfers in Appliances:

- Appliances transfer energy to perform work, such as heating, lighting, or moving something.
- The amount of energy transferred depends on the power rating of the appliance and how long it is used.
  - Formula:
- $E = Pt$   
Where:
  - $E$  = energy transferred (joules, J),
  - $P$  = power (watts, W),
  - $t$  = time (seconds, s).

### The National Grid:

- The **National Grid** distributes electricity from power stations to homes and businesses.
- **Step-up transformers** increase the potential difference to reduce energy losses during transmission, and **step-down transformers** lower it for safe domestic use.

### Static Electricity

#### Static Charge:

- When two insulating materials are rubbed together, electrons move from one material to another, causing one material to become **negatively charged** (gains electrons) and the other to become **positively charged** (loses electrons).
- **Like charges repel**, and **opposite charges attract**.

## Electric Fields:

- **Electric fields** are created around charged objects. Other charges in the field experience a force.
- The strength of the electric field is strongest close to the charged object and weakens with distance.
- **Field lines:**
  - Field lines point **away** from positive charges and **toward** negative charges.
  - The closer the field lines, the stronger the field.

## Field Around a Single Charge:

- **Positive charge:** The field lines radiate **outward** from the charge.
- **Negative charge:** The field lines point **inward** toward the charge.

## Field Between Two Charges:

- **Two like charges** (e.g., both positive or both negative): The field lines **repel** each other. Between the two charges, the lines bend outward, showing a region of weaker field where the charges cancel each other out.
- **Two opposite charges** (positive and negative): The field lines move **from the positive charge to the negative charge**. This represents the attraction between opposite charges, with the lines curving toward the negative charge.

## Field Strength:

- The strength of the electric field depends on the **distance from the charge:**
  - **Closer** to the charge: The field is **stronger** (denser field lines).
  - **Farther away:** The field becomes **weaker** (field lines are more spread out).