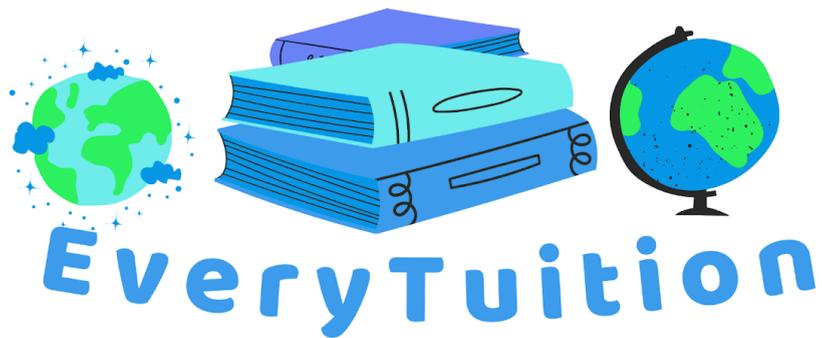


EveryTuition Revision- [etrevision.co.uk](http://etrevision.co.uk)

Connect With A Tutor: [everytuition.org](http://everytuition.org)

# GCSE Physics Topic 2 AQA: Electricity

Exam Questions/Mock Exam Questions



**Questions For Foundation, Higher, and Triple Science ([scroll down for questions for higher and triple science only](#)):**

(It would still be recommended to answer the foundation tier questions for triple science and higher tier to ensure you have good understanding).

**Q1.**

Jack is revising electrical circuits.

State the unit of current.

---

[1]

**Q2.**

Harry builds a simple circuit.

(a) State the equation linking current, charge and time.

---

[1]

(b) A current of 2 A flows for 30 s. Calculate the charge that flows.

---

---

[2]

[Total: 3 marks]

**Q3.**

Ben investigates potential difference.

(a) State the unit of potential difference.

---

[1]

(b) Suggest one piece of equipment used to measure potential difference.

---

[1]

[Total: 2 marks]

**Q4.**

Daniel studies resistance.

State the equation linking potential difference, current and resistance.

---

[1]

**Q5.**

Oliver connects a 12 V supply to a 6  $\Omega$  resistor.

Calculate the current in the circuit.

---

---

[2]

**Q6.**

Ethan looks at current in a series circuit.

(a) State how current is shared in a series circuit.

---

[1]

(b) State how potential difference is shared in a series circuit.

---

[1]

[Total: 2 marks]

**Q7.**

Sam builds a parallel circuit.

Explain how current is shared in a parallel circuit.

---

---

[2]

**Q8.**

Charlie investigates resistance.

(a) State the equation linking resistance, resistivity, length and area of a wire.

---

[1]

(b) State one factor (other than length and area) that affects resistance of a wire.

---

[1]

[Total: 2 marks]

**Q9.**

Noah studies resistors.

Explain what happens to the total resistance when two resistors are connected in parallel.

---

---

---

[3]

**Q10.**

Jacob learns about charge flow.

(a) State the unit of charge.

---

[1]

(b) A current of 0.5 A flows for 2 minutes. Calculate the charge.

---

---

---

[3]

[Total: 4 marks]

**Q11.**

William investigates power in electrical devices.

(a) Write the equation linking power, current and potential difference.

---

[1]

(b) A kettle works at 230 V with a current of 8 A. Calculate the power.

---

---

---

[3]

[Total: 4 marks]

**Q12.**

Alex looks at electrical appliances.

Explain what is meant by the term “power rating” of an appliance.

---

---

[2]

**Q13.**

Luke studies energy transfer.

(a) State the equation linking energy, power and time.

---

[1]

(b) A 60 W light bulb is on for 5 hours. Calculate the energy transferred in kWh.

---

---

---

[3]

[Total: 4 marks]

**Q14.**

James is revising mains electricity.

(a) State the potential difference of the UK mains supply.

---

[1]

(b) State the frequency of the UK mains supply.

---

[1]

[Total: 2 marks]

**Q15.**

Tom draws the wiring diagram of a plug.

(a) Name the colour of the live wire.

---

[1]

(b) State the function of the earth wire.

---

---

[2]

(c) Explain why the earth wire is a safety feature.

---

---

---

[3]

[Total: 6 marks]

## Higher Tier

### Q16.

Jack investigates current in a circuit.

(a) State the equation linking current, charge and time.

---

[1]

(b) A current of 3.5 A flows for 2 minutes. Calculate the charge that flows.

---

---

---

[3]

[Total: 4 marks]

### Q17.

Harry is measuring resistance.

(a) State the equation linking potential difference, current and resistance.

---

[1]

(b) A resistor has a potential difference of 12 V across it and a current of 0.5 A. Calculate its resistance.

---

---

---

[3]

[Total: 4 marks]

**Q18.**

Ben investigates I–V characteristics.

(a) Sketch the shape of the I–V graph for a filament lamp.

---

---

[2]

(b) Explain why the shape of the graph is not a straight line.

---

---

---

[3]

[Total: 5 marks]

**Q19.**

Daniel is learning about Ohmic conductors.

Explain what is meant by an Ohmic conductor.

---

---

---

[2]

**Q20.**

Oliver investigates resistors in series and parallel.

(a) Describe what happens to the total resistance when two resistors are connected in series.

---

---

[2]

(b) Explain what happens to the total resistance when two resistors are connected in parallel.

---

---

---

[3]

[Total: 5 marks]

**Q21.**

Ethan studies diodes.

(a) Draw the symbol for a diode.

---

[1]

(b) Explain how a diode behaves in a circuit.

---

---

[2]

[Total: 3 marks]

**Q22.**

Sam investigates charge.

A charge of 240 C passes through a lamp in 2 minutes.

Calculate the current.

---

---

---

[3]

**Q23.**

Charlie studies the National Grid.

(a) Explain why transformers are used in the National Grid.

---

---

---

[3]

(b) State whether step-up or step-down transformers are used at:

- The power station → \_\_\_\_\_
- Homes → \_\_\_\_\_

[2]

[Total: 5 marks]

**Q24.**

Noah investigates the heating effect of a resistor.

(a) State the equation linking power, current and resistance.

---

[1]

(b) A current of 4 A flows through a 12  $\Omega$  resistor. Calculate the power.

---

---

---

[3]

[Total: 4 marks]

**Q25.**

Jacob is studying energy transfer.

A kettle is rated at 2.2 kW and is used for 3 minutes.

Calculate the energy transferred.

---

---

---

[3]

**Q26.**

William investigates alternating and direct current.

(a) Describe the difference between alternating current (a.c.) and direct current (d.c.).

---

---

[2]

(b) State one example of a source of a.c. and one source of d.c.

a.c. source: \_\_\_\_\_

d.c. source: \_\_\_\_\_

[2]

[Total: 4 marks]

**Q27.**

Alex learns about mains electricity.

State:

(a) The frequency of UK mains electricity.

\_\_\_\_\_

[1]

(b) The potential difference of UK mains electricity.

\_\_\_\_\_

[1]

[Total: 2 marks]

**Q28.**

Luke connects a lamp and a variable resistor in series.

Explain what happens to the brightness of the lamp when the resistance is increased.

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

[3]

**Q29.**

James investigates charge flow.

A current of 0.75 A flows through a circuit for 200 s.

Calculate the charge that flows.

---

---

---

[3]

**Q30.**

Tom builds a model circuit with a thermistor.

(a) State what happens to the resistance of the thermistor as temperature increases.

---

[1]

(b) Suggest one use of a thermistor in everyday life.

---

[1]

[Total: 2 marks]

**Q31.**

Jack studies energy transfer in electrical appliances.

(a) State the equation linking energy, charge and potential difference.

---

[1]

(b) A charge of 500 C flows through a potential difference of 9 V. Calculate the energy transferred.

---

---

---

[3]

[Total: 4 marks]

**Q32.**

Harry is studying electrical safety.

Explain why the earth wire is a safety feature in appliances with a metal case.

---

---

---

[3]

**Q33.**

Ben is using fuses.

State how a fuse works when too much current flows through a circuit.

---

---

[2]

**Q34.**

Daniel measures power.

An electric heater is connected to a 230 V supply. The current is 5 A.

(a) Calculate the power of the heater.

---

---

---

[3]

(b) State one energy transfer that takes place in the heater.

---

[1]

[Total: 4 marks]

**Q35.**

Oliver is looking at resistors.

(a) Sketch the I–V graph for a fixed resistor at constant temperature.

---

---

[2]

(b) Explain why the graph has this shape.

---

---

[2]

[Total: 4 marks]

**Q36.**

Ethan tests a filament lamp.

(a) Sketch the I–V graph for a filament lamp.

---

---

[2]

(b) Explain the behaviour of resistance as current increases.

---

---

---

[3]

[Total: 5 marks]

**Q37.**

Sam investigates LEDs.

State one advantage of LEDs compared to filament lamps.

---

---

[2]

**Q38.**

Charlie measures current in a parallel circuit.

A circuit has two identical branches. A total current of 6 A flows.

(a) State the current in each branch.

---

[1]

(b) Explain your answer.

---

---

[2]

[Total: 3 marks]

**Q39.**

Noah is revising electricity equations.

(a) Write the equation linking energy, power and time.

---

[1]

(b) A television has a power rating of 120 W and is on for 10 hours. Calculate the energy transferred in kWh.

---

---

---

[3]

[Total: 4 marks]

**Q40.**

Jacob is studying electrical safety.

Explain why circuit breakers are safer than fuses.

---

---

---

[3]

## Triple Science

**Q41.**

William investigates resistivity.

(a) State the equation linking resistance, resistivity, length and area.

---

[1]

(b) Explain how increasing the cross-sectional area of a wire affects its resistance.

---

---

[2]

[Total: 3 marks]

**Q42.**

Alex investigates superconductors.

Explain what is meant by a superconductor.

---

---

---

[3]

**Q43.**

Luke measures the heating effect of current.

State two disadvantages of resistors heating up when current flows.

---

---

[2]

**Q44.**

James studies alternating current.

(a) Sketch the shape of a graph showing potential difference against time for alternating current.

---

---

[2]

(b) Explain how the graph would look for direct current.

---

---

[2]

[Total: 4 marks]

**Q45.**

Tom investigates transformers.

(a) Write the equation linking potential difference and number of turns for the primary and secondary coils of a transformer.

---

[1]

(b) A transformer has 500 turns on the primary coil and 100 turns on the secondary coil. The primary potential difference is 230 V. Calculate the secondary potential difference.

---

---

---

[3]

[Total: 4 marks]

**Q46.**

Jack studies efficiency in the National Grid.

Explain how high-voltage transmission reduces energy loss.

---

---

---

[3]

**Q47.**

Harry investigates step-up and step-down transformers.

State the purpose of each type of transformer in the National Grid.

Step-up: \_\_\_\_\_

Step-down: \_\_\_\_\_

[2]

**Q48.**

Ben investigates power in terms of current and resistance.

Derive the equation  $P=I^2R$  from the equations you have studied.

---

---

---

[3]

**Q49.**

Daniel studies current in different materials.

Explain why metals are good conductors of electricity.

---

---

---

[3]

**Q50.**

Oliver investigates fuses.

A hairdryer works at 230 V and has a power rating of 2000 W.

(a) Calculate the current in the hairdryer.

---

---

---

[3]

(b) State which fuse rating should be chosen: 3 A, 5 A, or 13 A.

---

[1]

[Total: 4 marks]

**Q51.**

Ethan studies resistance at different temperatures.

Explain why the resistance of a metal increases as temperature increases.

---

---

---

[3]

**Q52.**

Sam is researching potential difference.

Explain, in terms of energy, what potential difference means.

---

---

---

[3]

**Q53.**

Charlie investigates circuit design.

(a) Explain one advantage of using parallel circuits in household wiring.

---

---

[2]

(b) Explain one disadvantage of series circuits in household wiring.

---

---

[2]

[Total: 4 marks]

**Q54.**

Noah works out efficiency.

A transformer has an input power of 500 W and an output power of 480 W.

Calculate the efficiency of the transformer.

---

---

---

[3]

**Q55.**

Jacob studies alternating current.

Explain why alternating current is used in the National Grid instead of direct current.

---

---

---

[3]